

DAY-3 DESIGN LIBRARY CELL USING MAGIC LAYOUT AND NGSPICE CHARACTERIZATION.

1. CMOS inverter ngspice simulations

1: Spice deck

- This image shows a SPICE deck (simulation input file) and a CMOS inverter circuit used for analog simulation.

Left Side – SPICE Deck:

- Netlist Description:
 - M1 is a PMOS transistor ($W=0.375\mu\text{m}$, $L=0.25\mu\text{m}$).
 - M2 is an NMOS transistor (same dimensions).
- Capacitive Load: load of 10fF between output and ground.
- Voltage Sources:
 - Vdd provides 2.5V to power rail.
 - Vin is the input voltage source swept from 0V to 2.5V in steps of 0.05V.
- Simulation Commands:
 - .op: Operating point analysis.
 - .dc: DC sweep of Vin.

Right Side – Circuit Diagram:


- CMOS inverter using:
 - M1 (PMOS) on top, connected to Vdd.
 - M2 (NMOS) at the bottom, connected to Vss.
- Output (out) node connected to a 10fF capacitor (load).
- Vin drives the gates of both transistors.

SPICE deck

```
*** MODEL Descriptions ***
*** NETLIST Description ***
M1 out in vdd vdd pmos W=0.375u L=0.25u
M2 out in 0 0 nmos W=0.375u L=0.25u


cload out 0 10f

 Vdd vdd 0 2.5
Vin in 0 0.5
*** SIMULATION Commands ***
.op
.dc Vin 0 2.5 0.05
*** .include tsmc_025um_model.mod ***
.LIB "tsmc_025um_model.mod" CMOS MODELS
.end
```




 2: Spice Simulation & Switching Threshold


- Where both the nmos and pmos are of equal width.




- When width of pmos is thrice to nmos

 

 
- Switching Threshold is the point where the straight line and the curve meets it determines the ON and OFF for transistors.



- Switching Threshold of two graphs


 


- DC characteristics of nmos and pmos.

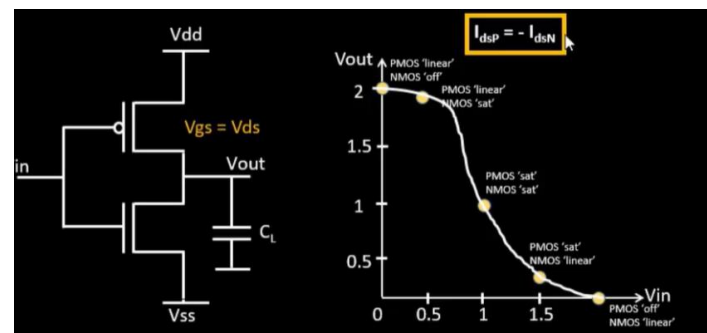


 
 
3: Spice Simulation & Switching Threshold

- The graph Time vs Voltage will be plotted here from where we can calculate the rise and fall delay




   2. Inception of Layout and CMOS fabrication process


- At each step changes are done such that to achieve a proper fabrication process and make it ready for the further step.
- We select a p type substrate creating a region for nmos and pmos.
- We use SiO_2 and Si_3N_4 layer for isolation
- A photoresist is used which is a light-sensitive material applied to a silicon wafer to define patterns for subsequent processing steps such as etching or doping.
- UV rays are used to etch the area which is exposed.
- We use n type and p type doping substances for creating the well.
- Create Active regions




- Formation of N-well and P-well

 


- Formation of gate terminal

 


- Lightly doped drain (LDD) formation

 


- Source and drain formation

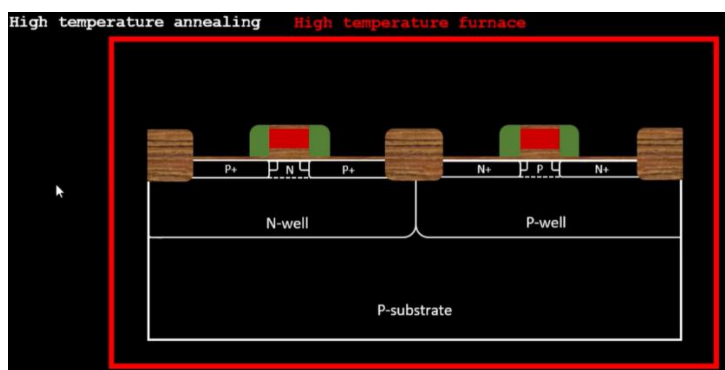

- Local interconnect formation

 

- Higher level metal formation

 

- Final fabrication of CMOS is as below

